

CONFIDENTIAL

CONFIDENTIAL

50X1-HUM

	<u>Page</u>
4. Duhamel's Theorem for Envelopes	33
5. Calculation of Envelopes for a Single Pulse	38
6. Comparison of Calculations Using Accurate and Simplified Equations	39
Chapter III. Transient Phenomena in Idealized Selective Four-Terminal Networks	
1. Statement of the Problem	48
2. Nondistorting Four-Terminal Networks	49
3. Resonance Amplifier Where $\eta = \infty$	53
4. Band Filters	62
5. Ideal Band Filter	69
Chapter IV. Transient Phenomena in Resonance Amplifiers	
1. Brief Data on Frequency and Phase Characteristics	76
2. Connecting a Constant Voltage	83
3. Connecting a Harmonic Voltage of Resonant Frequency	86
4. Connecting a Voltage Detuned From Resonance	90
5. Connecting a Voltage With a Linearly Increasing Amplitude	97
6. Disconnecting a Constant Voltage	100
7. Disconnecting a Harmonic Voltage	103
8. Path of an Impulse With a Triangular Envelope	108
Chapter V. Transient Phenomena in Band Amplifiers (First Type)	
1. Brief Data on Frequency and Phase Characteristics	111
2. Connecting a Constant Voltage	120
3. Connecting a Harmonic Voltage of Resonant Frequency	125
4. Connecting a Voltage Detuned From Resonance	134
5. Connecting a Voltage With a Linearly Increase Amplitude	137
6. Disconnecting a Harmonic Voltage	141

- 2 -

CONFIDENTIAL

CONFIDENTIAL

CONFIDENTIAL

CONFIDENTIAL

50X1-HUM

	<u>Page</u>
Chapter VI. Transient Phenomena in Band Amplifiers (Second Type)	
1. Brief Data on Frequency and Phase Characteristics	143
2. Connecting a Constant Voltage	150
3. Connecting a Harmonic Voltage	155
Chapter VII. Transient Phenomena in Band Amplifiers With a Three-Circuit Filter	
1. Brief Data on Frequency and Phase Characteristics	162
2. Connecting Constant and Harmonic Voltages	168
Chapter VIII. Transient Phenomena With Jumps in Phase and Frequency	
1. Transient Phenomena With a Jump in Phase	173
2. Transient Phenomena With a Jump in Frequency	177
3. Transient Phenomena in a Discriminator	184
Chapter IX. Transient Phenomena in a Resistance-Coupled Amplifier	
1. Discussion of Original Equations	194
2. Transient Phenomena Attributed to Input Capacitance	197
3. Transient Phenomena Attributed to Distributed Capacitance	199
Appendix Table of Symbolic Equations and Solutions	205
Bibliography	206

- E N D -

- 3 -

CONFIDENTIAL

CONFIDENTIAL